


You must show **all** your work! Answers without supporting work will not be given credit.

All problems are inspired by our *Introduction to Logic Design 3rd Edition* text. Any submissions which are not clear and use a respectable amount of space will **NOT** be considered.

This assignment is worth 10.0 points.

Name: Sebastian Garcia

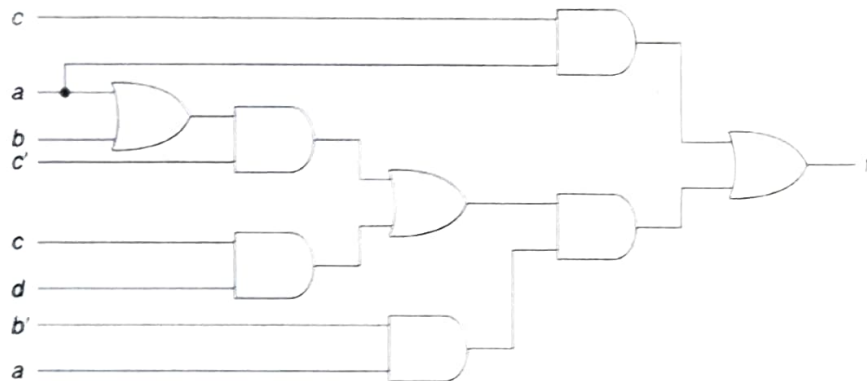1. Consider the following circuit and provide analysis as indicated. (1.25 Points)



Give your answers in terms of Δ .

- (a) How long until the circuit is stable if complemented variables are available?

Answer: 5 Δ


- (b) Which variable(s) is(are) on the longest path to f , if only uncomplemented variables are available?

Answer: a, b

- (c) How long until the circuit is stable after input a changes (there is only one answer)?

Answer: 20

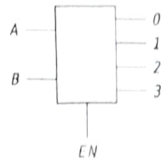2. Using three (3) of the following 2-to-4 active-high enabled, active-high output binary decoders, build a 3-to-8 active-high output binary decoder. (1.25 Points)



A 2-to-4 active-high enabled, active-high output binary decoder.


Your decoder should have inputs x, y, z and output lines 0, 1, 2, 3, 4, 5, 6, 7:

x, y, z inputs are select lines for output,


Your decoder's eight output should be ascending, top-to-bottom,

Your decoder does not require an enable, and

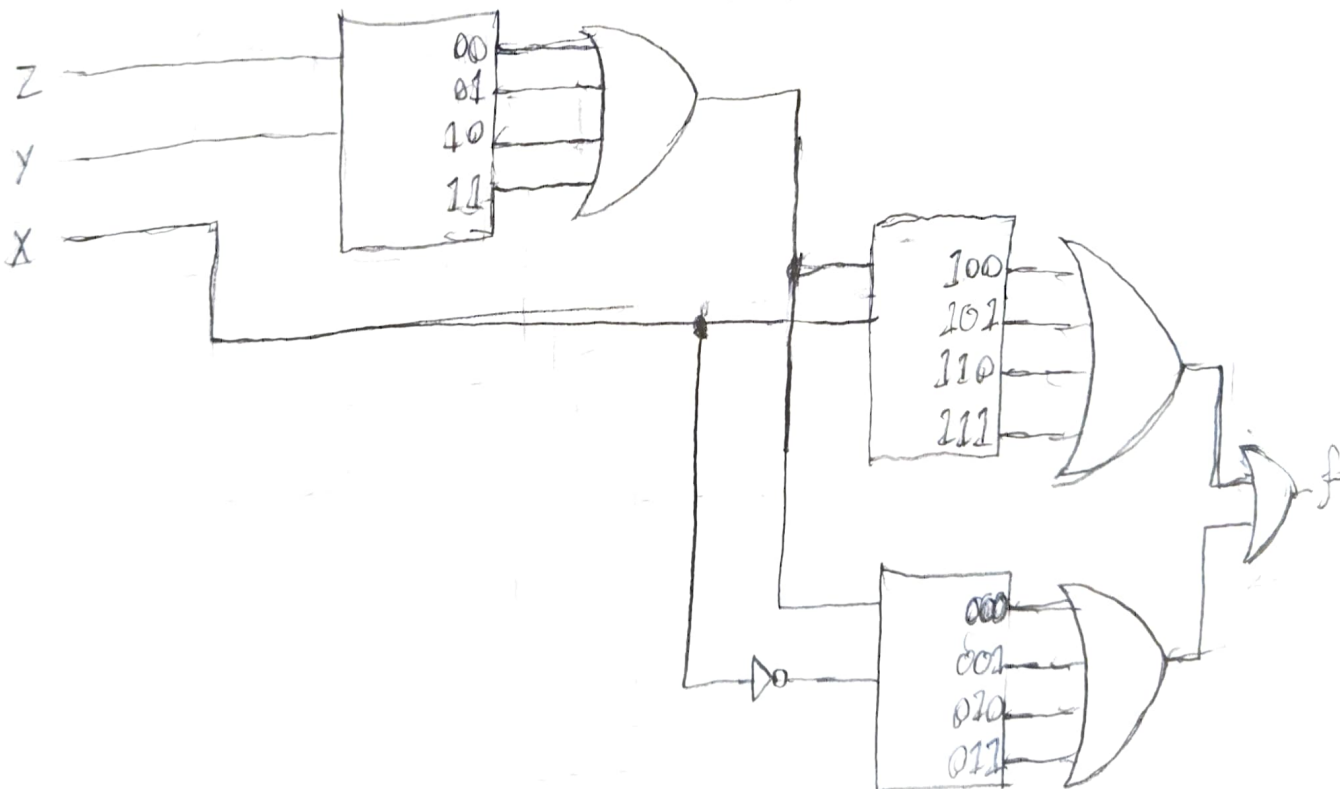You may assume you can access a low or high signal (0 or 1) as needed.




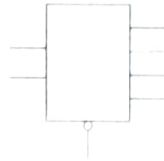3. Using two (2) of the following decoders and any number of OR and NOT gates, implement a **one-bit full binary adder**. (1.25 Points)



A 2-to-4 active-low enabled, active-high output binary decoder.

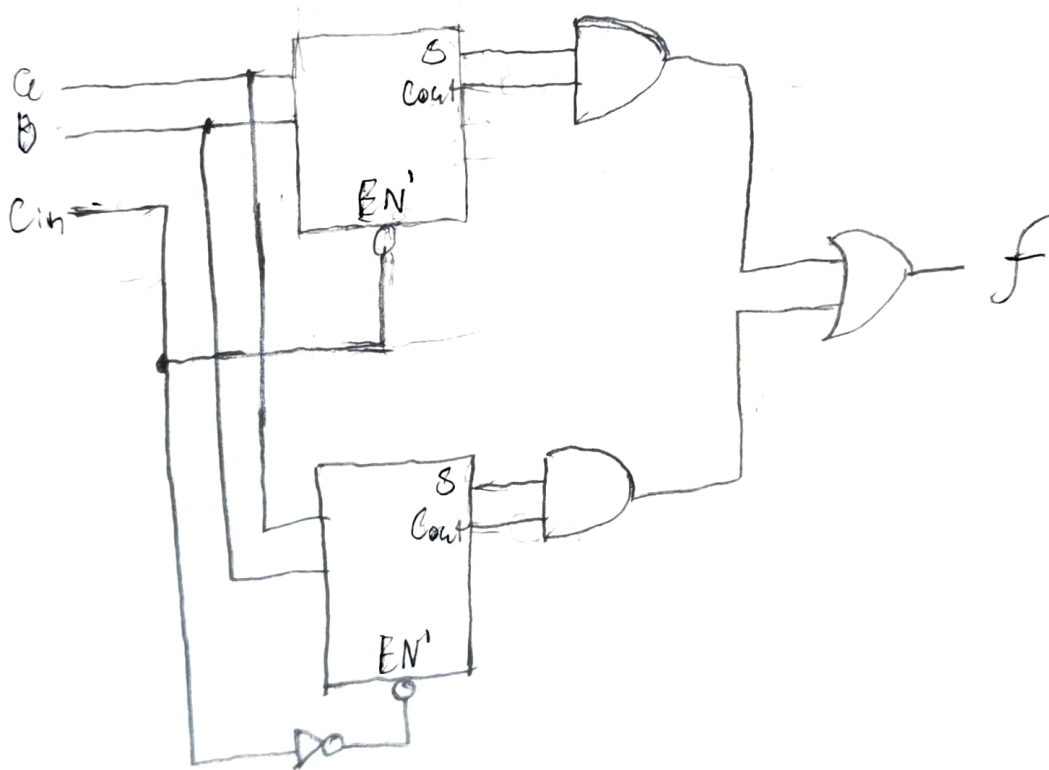
Your adder should have the standard inputs a, b, c_{in} and the standard outputs s, c_{out} . See Figure 1.2 for reminder and Table 1.5 for an explanation of behavior (page 10 from our text).





Cont.

4. Using exactly seven (7) two-way MUX, implement the following function. You should also attempt to use **row-pairing** and exactly three (3) two-way MUX. (1.25 Points)

$$f(x, y, z) = \Sigma m(0, 1, 3, 7)$$

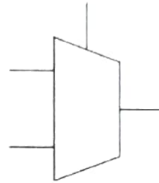

A two-way MUX.

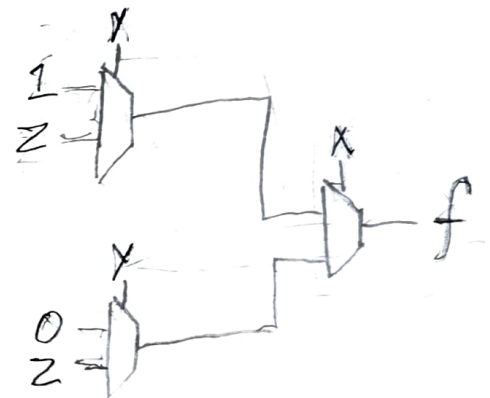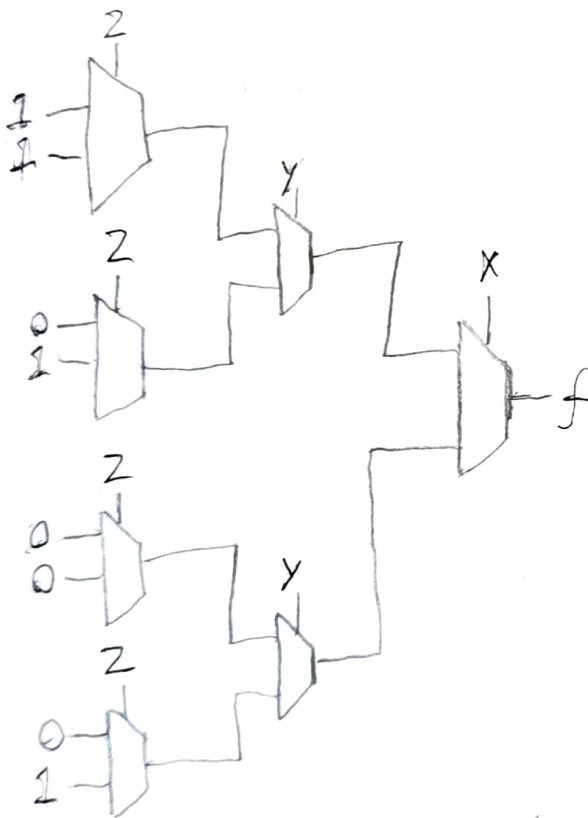

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$f = 1$ for (0,0,0), (0,0,1)
 $f = 2$ for (0,1,0), (0,1,1)
 $f = 0$ for (1,0,0), (1,0,1), (1,1,0)
 $f = 2$ for (1,1,1)

Cont.


5. For the following functions, program a ROM and PLA; a separate function will be provided for a PAL.
(3.75 points)

$$F(A, B, C, D) = \Sigma m(0, 1, 2, 3, 9, 10, 13, 14)$$


$$G(A, B, C, D) = \Sigma m(0, 1, 8, 9, 10, 12, 13, 14)$$

$$H = AD' + A'B'C + ABC$$

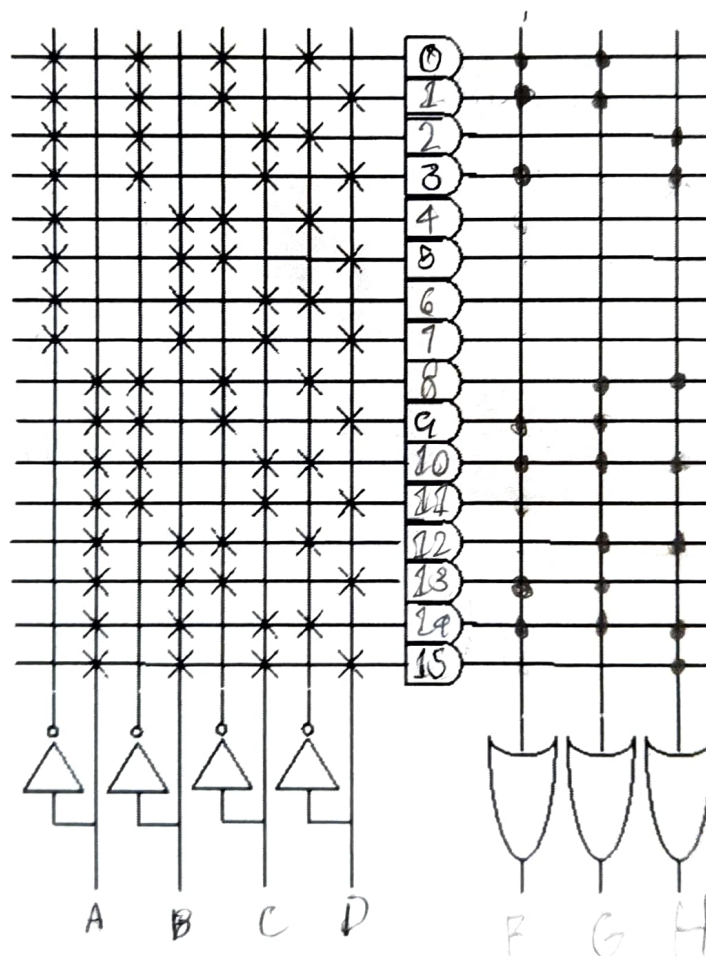- (a) Label the AND gates corresponding to minterms (0-15) and "program" functions F, G, H . (1.25 points)



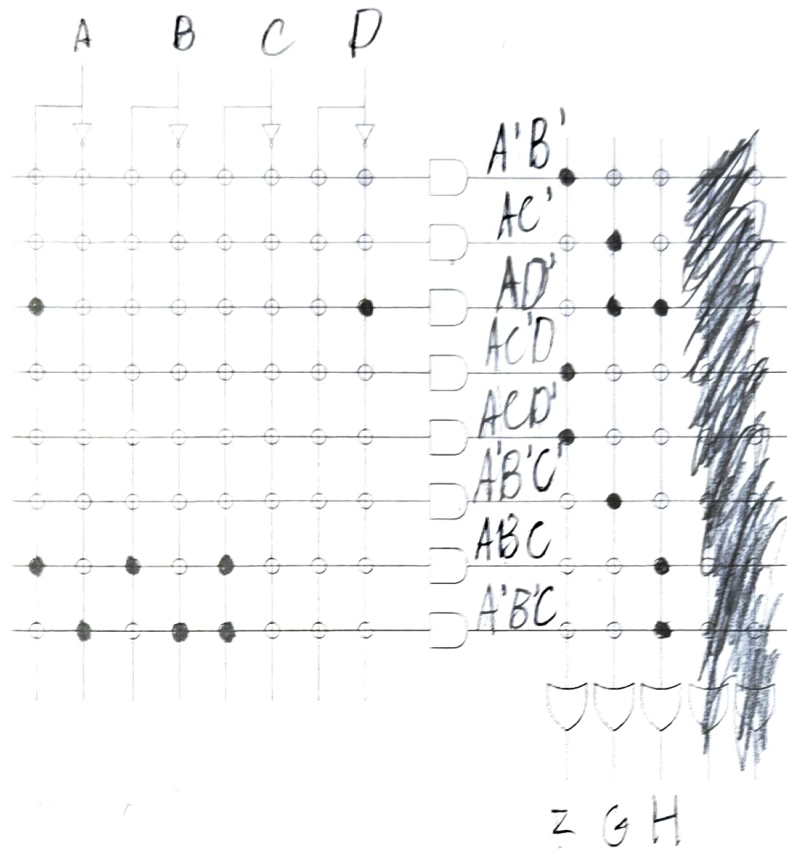- (b) Using the functions from the previous section, encode F , G , and H using the following PLA. You will need to share terms between functions. Label each line with its product term. (1.25 points)




$$F = A'B' + AC'D + ACD'$$

$$G = AD' + AC' + A'B'C'$$

$$H = AD' + A'BC + ABC$$

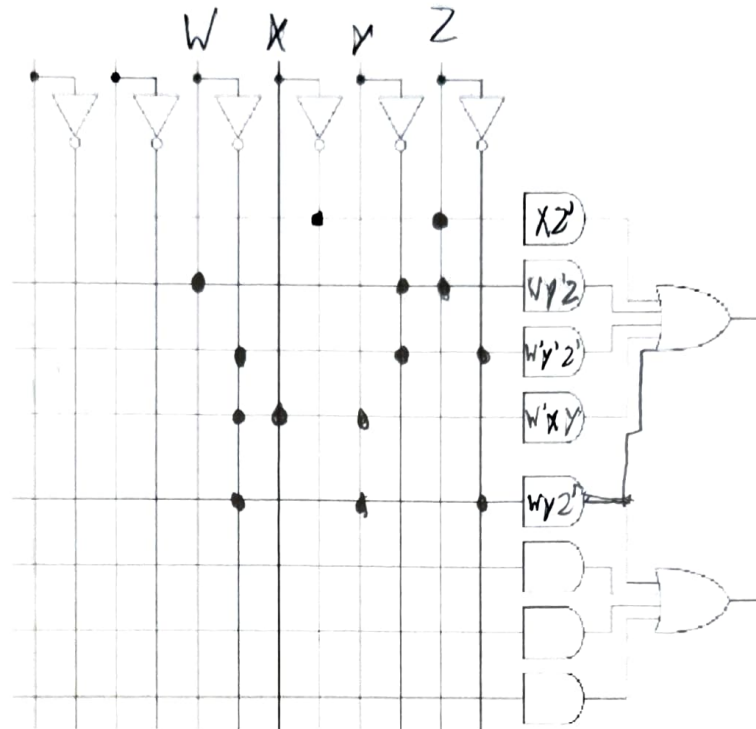
- (c) Encode the function $f(w, x, y, z) = \sum m(0, 1, 3, 4, 7, 6, 9, 11, 10, 13, 14)$. You must label your product terms and use the left-most and top-most input/output lines for any required feedback for credit. (1.25 points)



$$f = XZ' + WY'Z + W'Y'Z' + W'XY + WYZ' + WYZ$$

6. Draw both the state diagram and complete the timing sequence as x changes until you have no distinct state information remaining. (1.25 points)

q	q		z	
	$x=0$	$x=1$	$x=0$	$x=1$
A	A	B	1	0
B	C	D	0	0
C	A	B	0	0
D	C	D	1	0

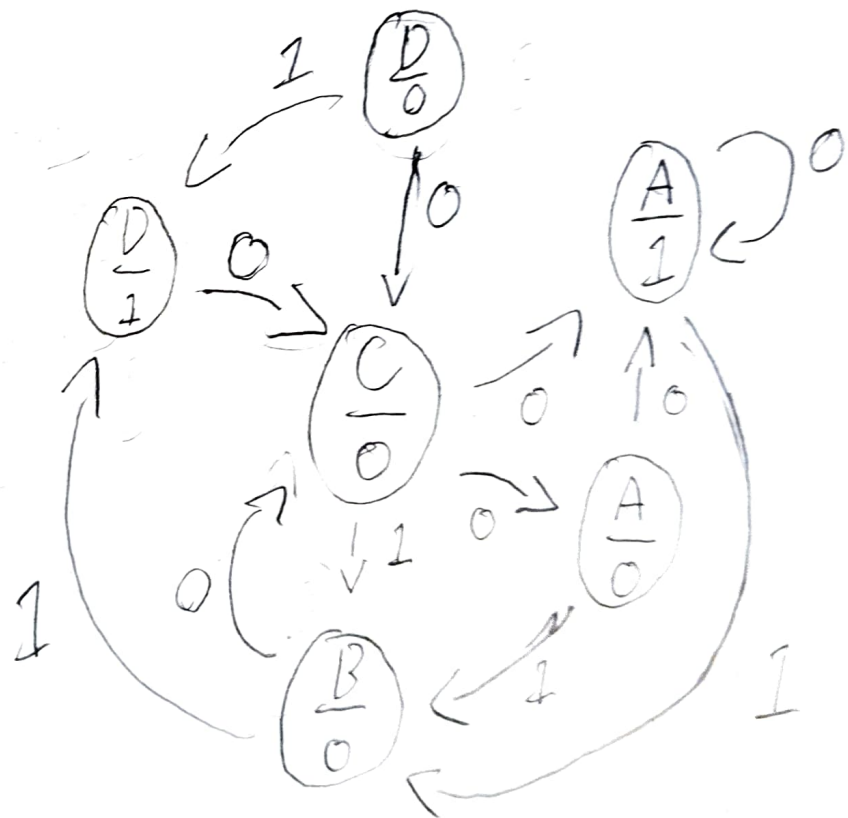

x	1	0	1	1	1	0
q	?	B	C	B	D	C
z	0	0	0	0	1	0

The End.